

Cpr E 381: Computer Organization and Assembly-Level Programming

Project Part 2 Report

Team Members: __Noah Ross_____

__Alex Brown_____


Project Teams Group #: _____**5**_____

Refer to the highlighted language in the project 1 instruction for the context of the following questions.


[1.a] Come up with a global list of the datapath values and control signals that are required during each pipeline stage.

IF → ID	ID → EX	EX → Mem	Mem → WB
Instructions	Immediate	ALU out	ALU out
jv	RS	RT (write data)	mem out
halt delay	RT	RD1	RD1
JalWriteData	shamt	RD2	RD2
	branch	jv	jv
	RD 1	Reg Dst	Reg Dst
	RD 2	Reg Wr	Reg Wr
	jv	Mem Write	Mem to Reg
	ALU ctrl	Mem to Reg	halt
	Reg Dst	Mem Read	
	Reg Wr	halt	
	ALU src		
	Mem Write		
	Mem to Reg	Proc Hw	5%
	Mem Read	in lecture	5%
	Halt delay	Hw	5%
	jv	labs	10%
Proj 2	in.	Term Proj	30%
fetch mID, slt in EX?		Exams	15%
		✓	15%

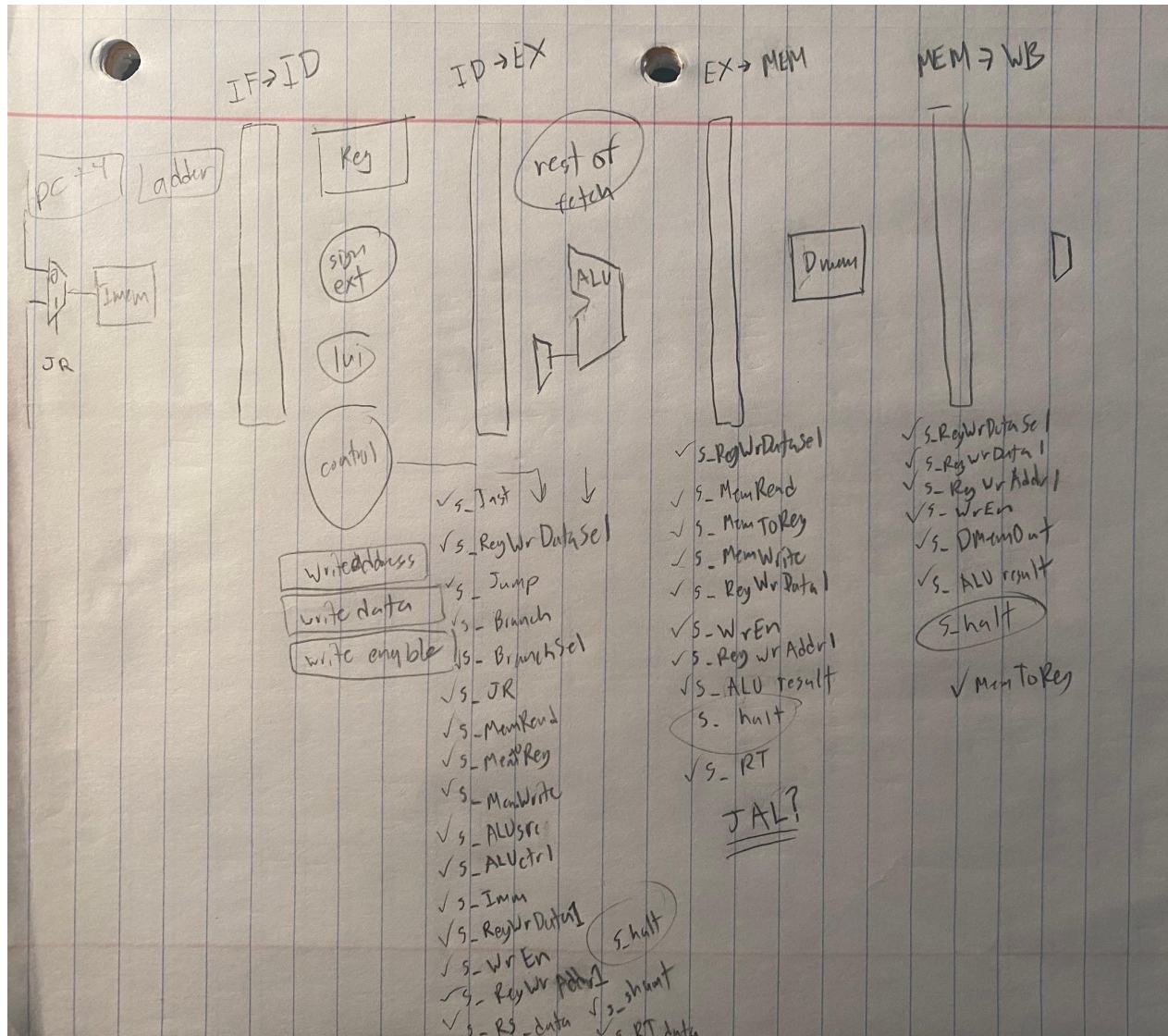[1.b.ii] High-level schematic drawing of the interconnection between components.



 [1.c.i] Include an annotated waveform in your writeup and provide a short discussion of result correctness.



```

addi $t3, $0, 08210
addiu $t2, $0, 248
nop
nop
nop
add $t1, $t2, $t3
nop
nop
nop
addu $t1, $t1, $0


```

1
2
3
4
5
6

I checked the entirety of the program by comparing it to what mars.sim had and by checking the Inst and RegWrData to their expected values. Everything matched

[1.c.ii] Include an annotated waveform in your writeup of two iterations or recursions of these programs executing correctly and provide a short discussion of result correctness. In your waveform and annotation, provide 3 different examples (at least one data flow and one control flow) of where you did not have to use the maximum number of NOPs.

#1

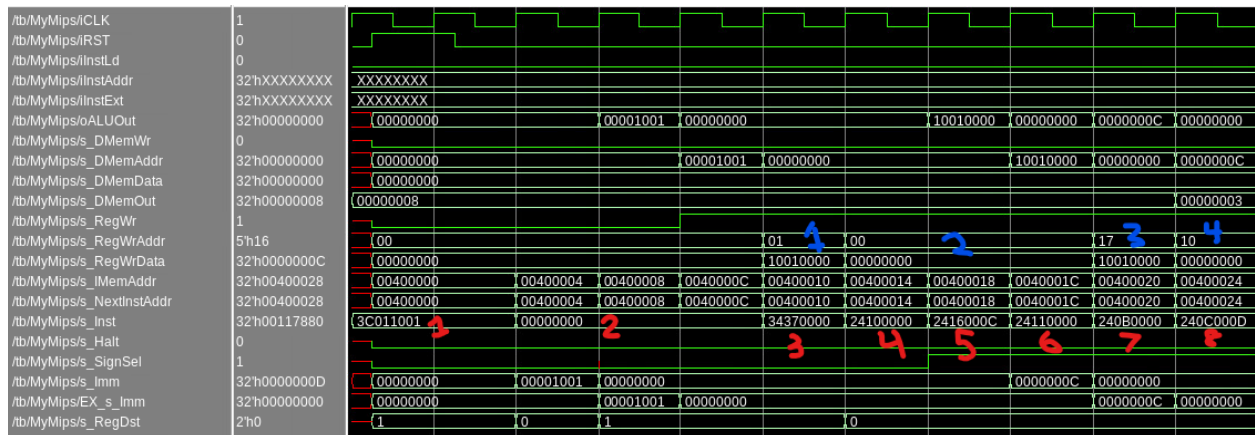

```
[inst #1] lui $1,4097
Register Write to Reg: 0x01 Val: 0x10010000 } → 1
[inst #2] sll $0,$0,$0
Register Write to Reg: 0x00 Val: 0x00000000 } → 2
[inst #3] sll $0,$0,$0
Register Write to Reg: 0x00 Val: 0x00000000 }
[inst #4] sll $0,$0,$0
Register Write to Reg: 0x00 Val: 0x00000000 }
[inst #5] ori $23,$1,0
Register Write to Reg: 0x17 Val: 0x10010000 → 3
[inst #6] addiu $16,$0,0
Register Write to Reg: 0x10 Val: 0x00000000 → 4
[inst #7] addiu $22,$0,12
Register Write to Reg: 0x16 Val: 0x00000000 → 5
[inst #8] addiu $17,$0,0
Register Write to Reg: 0x11 Val: 0x00000000 → 6
[inst #9] addiu $11,$0,0
Register Write to Reg: 0x0B Val: 0x00000000 → 7
[inst #10] addiu $12,$0,13
Register Write to Reg: 0x0C Val: 0x00000000 → 8
[inst #11] sll $15,$17,2
Register Write to Reg: 0x0F Val: 0x00000000
```

For most of these instructions, no nops were required because the beginning of our bubble sort is just loading the initial values into different registers.

#2

```
lw $t0, 0($t7)           #load numbers[j]
lw $t1, 4($t7)           #load numbers[j+1]
nop
nop
nop

slt $t2, $t0, $t1        #if t0 < t1
```

/tb/MyMips/s_RegWr	1						
/tb/MyMips/s_RegWrAddr	5'h16	0F	00			08	09
/tb/MyMips/s_RegWrData	32'h0000000C	10010000	00000000			00000008	00000064
/tb/MyMips/s_IMemAddr	32'h00400028	00400048	0040004C	00400050	00400054	00400058	0040005C
/tb/MyMips/s_NextInstAddr	32'h00400028	00400048	0040004C	00400050	00400054	00400058	0040005C
/tb/MyMips/s_Inst	32'h00117880	8DE80000	8DE90004	00000000			0109502A

Lw \$t0 lw \$t1 nop x 3 slt

The lw \$t0 instruction requires no nops because the next instruction needs 3, so the instruction is given time to write back.

#3

```
addi $s1, $s1, 1          #increment t1
sub $s5, $s6, $s0         #subtract s0 from s6
nop
nop
nop
bne $s1, $s5, loop        #if s1 (counter for second loop)
```

/tb/MyMips/s_RegWr	1						
/tb/MyMips/s_RegWrAddr	5'h16	00				11	15
/tb/MyMips/s_RegWrData	32'h0000000C	00000000				00000001	0000000C
/tb/MyMips/s_IMemAddr	32'h00400028	00400084	00400088	0040008C	00400090	00400094	00400098
/tb/MyMips/s_NextInstAddr	32'h00400028	00400084	00400088	0040008C	00400090	00400094	00400098
/tb/MyMips/s_Inst	32'h00117880	22310001	02D0A822	00000000			1635FFE3

Addi sub nop x 3 bne

The addi \$s1 instruction requires no nops because the next instruction needs 3, so the instruction is given time to write back.

[1.d] Report the maximum frequency your software-scheduled pipelined processor can run at and determine what your critical path is (specify each module/entity/component that this path goes through).

FMax: 52.41mhz Clk Constraint: 20.00ns Slack: 0.92ns

Our critical path was the alu. The bit shifter and adder and or/ander slow things down greatly and was, therefore, the critical path (the longest cycle). The path goes through a mux for ALU_B input and then the ALU, and then the Fetch Unit.


Total (ns)	Incr (ns)	Type	Element
0.000	0.000		launch edge time
3.089	3.089	R	clock network delay
3.321	0.232	uTco	reg_N:RT_Reg dffg:\G_NBit_REG:0:DFF s_Q
3.321	0.000	FF	CELL RT_Reg \G_NBit_REG:0:DFF s_Q q
4.139	0.818	FF	IC ALU_B_MUX \G_NBit_MUX:0:MUXI g_OR2 o_F~0 datad
4.264	0.125	FF	CELL ALU_B_MUX \G_NBit_MUX:0:MUXI g_OR2 o_F~0 combout
4.568	0.304	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:0:ADD g_AND2 o_F datab
4.918	0.350	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:0:ADD g_AND2 o_F combout
5.217	0.299	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:1:ADD g_OR o_F~0 dataa
5.641	0.424	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:1:ADD g_OR o_F~0 combout
5.894	0.253	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:2:ADD g_OR o_F~0 datad
6.019	0.125	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:2:ADD g_OR o_F~0 combout
6.267	0.248	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:3:ADD g_OR o_F~0 datad
6.392	0.125	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:3:ADD g_OR o_F~0 combout
6.820	0.428	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:4:ADD g_OR o_F~0 datad
6.945	0.125	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:4:ADD g_OR o_F~0 combout
7.195	0.250	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:5:ADD g_OR o_F~0 datad
7.320	0.125	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:5:ADD g_OR o_F~0 combout
7.571	0.251	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:6:ADD g_OR o_F~0 datad
7.696	0.125	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:6:ADD g_OR o_F~0 combout
7.945	0.249	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:7:ADD g_OR o_F~0 datad
8.070	0.125	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:7:ADD g_OR o_F~0 combout
8.321	0.251	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:8:ADD g_OR o_F~0 datad
8.446	0.125	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:8:ADD g_OR o_F~0 combout
8.705	0.259	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:9:ADD g_OR o_F~0 datac
8.986	0.281	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:9:ADD g_OR o_F~0 combout
9.244	0.258	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:10:ADD g_OR o_F~0 datac
9.525	0.281	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:10:ADD g_OR o_F~0 combout
9.780	0.255	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:11:ADD g_OR o_F~0 datac
10.061	0.281	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:11:ADD g_OR o_F~0 combout
10.314	0.253	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:12:ADD g_OR o_F~0 datad
10.439	0.125	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:12:ADD g_OR o_F~0 combout
10.689	0.250	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:13:ADD g_OR o_F~0 datad
10.814	0.125	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:13:ADD g_OR o_F~0 combout
11.207	0.393	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:14:ADD g_OR o_F~0 datad
11.332	0.125	FF	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:14:ADD g_OR o_F~0 combout

13.366	0.125	FF	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:19:ADD g_OR o_F~0 combout
13.618	0.252	FF	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:20:ADD g_OR o_F~0 datad
13.743	0.125	FF	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:20:ADD g_OR o_F~0 combout
13.991	0.248	FF	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:21:ADD g_OR o_F~0 datad
14.116	0.125	FF	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:21:ADD g_OR o_F~0 combout
14.374	0.258	FF	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:22:ADD g_OR o_F~0 datad
14.655	0.281	FF	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:22:ADD g_OR o_F~0 combout
14.911	0.256	FF	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:23:ADD g_OR o_F~0 datad
15.192	0.281	FF	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:23:ADD g_OR o_F~0 combout
15.443	0.251	FF	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:24:ADD g_OR o_F~0 datad
15.568	0.125	FF	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:24:ADD g_OR o_F~0 combout
15.823	0.255	FF	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:25:ADD g_OR o_F~0 datad
16.104	0.281	FF	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:25:ADD g_OR o_F~0 combout
16.360	0.256	FF	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:26:ADD g_OR o_F~0 datad
16.641	0.281	FF	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:26:ADD g_OR o_F~0 combout
16.892	0.251	FF	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:27:ADD g_OR o_F~0 datad
17.017	0.125	FF	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:27:ADD g_OR o_F~0 combout
17.266	0.249	FF	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:28:ADD g_OR o_F~0 datad
17.391	0.125	FF	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:28:ADD g_OR o_F~0 combout
17.642	0.251	FF	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:29:ADD g_OR o_F~0 datad
17.767	0.125	FF	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:29:ADD g_OR o_F~0 combout
18.154	0.387	FF	IC	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~6 datad
18.304	0.150	FR	CELL	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~6 combout
18.506	0.202	RR	IC	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~18 datad
18.661	0.155	RR	CELL	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~18 combout
18.866	0.205	RR	IC	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~19 datad
19.005	0.139	RF	CELL	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~19 combout
19.254	0.249	FF	IC	EX_Fetch_Unit branchSel o_F~0 datad
19.404	0.150	FR	CELL	EX_Fetch_Unit branchSel o_F~0 combout
19.677	0.273	RR	IC	Fetch_Unit_IF g_pcreg \G_NBit_REG:9:REGI s_Q~2 datad
19.944	0.267	RF	CELL	Fetch_Unit_IF g_pcreg \G_NBit_REG:9:REGI s_Q~2 combout
20.813	0.869	FF	IC	Fetch_Unit_IF g_MUX \G_NBit_MUX:20:MUXI g_OR2 o_F~0 datad
21.094	0.281	FF	CELL	Fetch_Unit_IF g_MUX \G_NBit_MUX:20:MUXI g_OR2 o_F~0 combout
21.321	0.227	FF	IC	Fetch_Unit_IF g_MUX \G_NBit_MUX:20:MUXI g_OR2 o_F~1 datad
21.446	0.125	FF	CELL	Fetch_Unit_IF g_MUX \G_NBit_MUX:20:MUXI g_OR2 o_F~1 combout
21.681	0.235	FF	IC	Fetch_Unit_IF g_MUX \G_NBit_MUX:20:MUXI g_OR2 o_F~2 datad
21.962	0.281	FF	CELL	Fetch_Unit_IF g_MUX \G_NBit_MUX:20:MUXI g_OR2 o_F~2 combout
21.962	0.000	FF	IC	Fetch_Unit_IF g_pcreg \G_NBit_REG:20:REGI s_Q d
22.066	0.104	FF	CELL	fetchIF:Fetch_Unit_IF PCreg:g_pcreg PCdffg:\G_NBit_REG:20:REGI s_Q


Data Required Path:

Total (ns) Trce (ns) Type Element

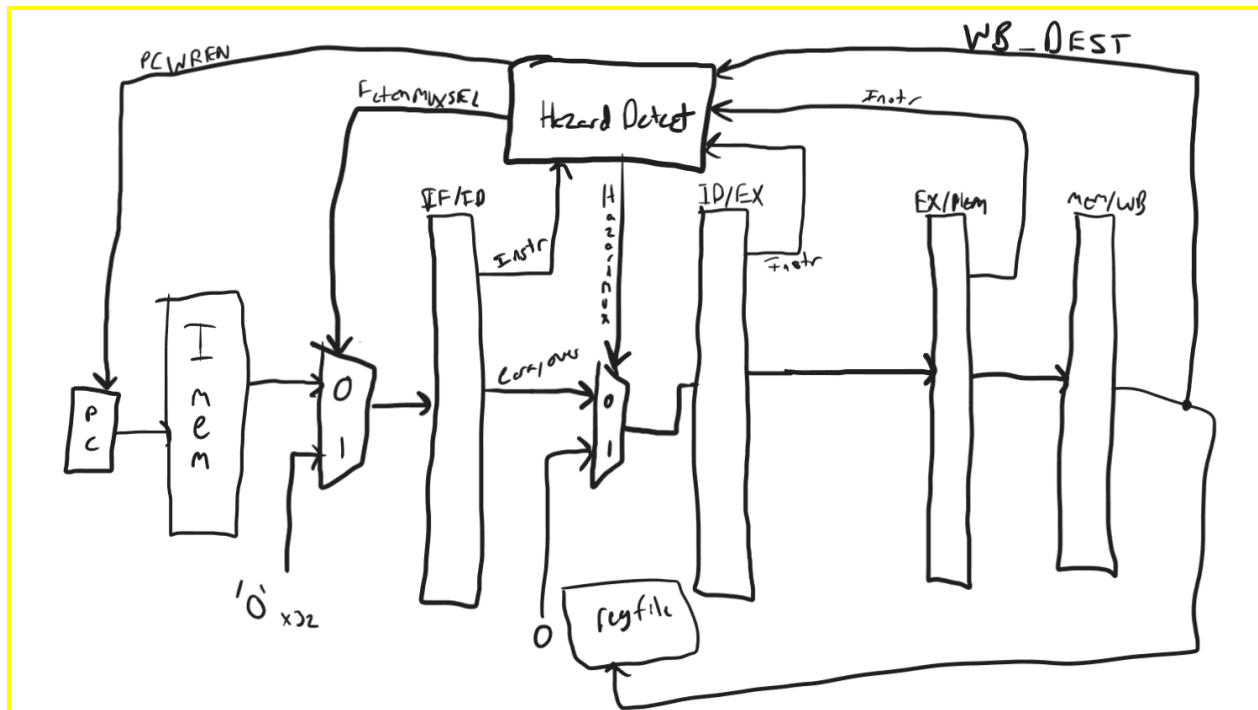[2.a.ii] Draw a simple schematic showing how you could implement stalling and flushing operations given an ideal N-bit register.



 [2.a.iii] Create a testbench that instantiates all four of the registers in a single design. Show that values that are stored in the initial IF/ID register are available as expected four cycles later, and that new values can be inserted into the pipeline every single cycle. Most importantly, this testbench should also test that each pipeline register can be individually stalled or flushed.



Our team didn't make a register for each stage; we made a register for each signal. This was incredibly time-consuming, and I would not do it this way next time, but we were learning what signals we needed one at a time, and that was one way to make it functional. For this reason, we don't have a test bench that can test 4 registers for their ability to carry data to the next clock cycle, but we can show you the cascading signals. The example is Write Enable: you can see it is 1 when it is created in EX, then 1 in the next cycle (MEM), then 1 in the cycle after that (WB). This way, we could physically see each signal where it was at and add and subtract signals with ease.

[2.b.i] list which instructions produce values and what signals (i.e., bus names) in the pipeline these correspond to.

Specifying Signals Specific to the instructions production as opposed to all the other signals that are at play, such as ones that lead aid in consumption.

- **Addi** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData, EX_s_Imm
- **Addiu** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData, EX_s_Imm
- **Andi** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData, EX_s_Imm
- **Lui** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData, EX_s_Imm, s_LUI
- **Lw** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_RegWrData, WB_s_DmemOut
- **Slti** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData, EX_s_Imm
- **Sw (value produced in dmem)** - MEM_s_MemWrite, MEM_s_RT, MEM_s_ALUresult
- **Xori** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData, EX_s_Imm
- **Ori** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData, EX_s_Imm
- **Addu** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **Sub** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **Subu** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **And** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **Or** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **Xor** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **Nor** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **Slt** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **Add** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **sll** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **Srl** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **Sra** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_ALUresult, WB_s_RegWrData
- **Jal** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_RegWrData, EX_s_PCp4
- **Bgezal** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_RegWrData, EX_s_PCp4
- **bgtzal** - WB_s_WrEn, WB_s_MemtoReg(set to 0), WB_s_RegWrData, EX_s_PCp4

[2.b.ii] List which of these same instructions consume values and what signals in the pipeline these correspond to.

Specifying Signals Specific to the instruction's consumption as opposed to all the other signals that are at play such as ones that lead aid in production.

- **Addi** - ID_s_instruction, EX_s_RS
- **Addiu** - ID_s_instruction, EX_s_RS
- **Andi** - ID_s_instruction, EX_s_RS
- **Lw (consumes from dmem)** - EX_s_RS
- **Sw** - ID_s_instruction, MEM_s_MemWrite
- **Beq** - ID_s_instruction, ID_s_PCp4
- **Bne** - ID_s_instruction, ID_s_PCp4
- **Xori** - ID_s_instruction, EX_s_RS
- **Ori** - ID_s_instruction, EX_s_RS
- **Bgez** - ID_s_instruction, EX_s_RT, EX_s_RS, ID_s_PCp4
- **Bgezal** - ID_s_instruction, EX_s_RT, EX_s_RS, ID_s_PCp4
- **Bgtz** - ID_s_instruction, EX_s_RT, EX_s_RS, ID_s_PCp4
- **Blez** - ID_s_instruction, EX_s_RT, EX_s_RS, ID_s_PCp4
- **Bltzal** - ID_s_instruction, EX_s_RT, EX_s_RS, ID_s_PCp4
- **Blitz** - ID_s_instruction, EX_s_RT, EX_s_RS, ID_s_PCp4
- **Addu** - ID_s_instruction, EX_s_RT, EX_s_RS
- **Sub** - ID_s_instruction, EX_s_RT, EX_s_RS
- **Subi** - ID_s_instruction, EX_s_RT, EX_s_RS
- **And** - ID_s_instruction, EX_s_RT, EX_s_RS
- **Or** - ID_s_instruction, EX_s_RT, EX_s_RS
- **Xor** - ID_s_instruction, EX_s_RT, EX_s_RS
- **Nor** - ID_s_instruction, EX_s_RT, EX_s_RS
- **Slt** - ID_s_instruction, EX_s_RT, EX_s_RS
- **Add** - ID_s_instruction, EX_s_RT, EX_s_RS
- **sll** - ID_s_instruction, EX_s_RT, EX_s_RS
- **srl** - ID_s_instruction, EX_s_RT, EX_s_RS
- **sra** - ID_s_instruction, EX_s_RT, EX_s_RS

Most of these instructions just use signals pertaining to where their data is to be consumed from. There is obviously a lot more that goes into it, but these are the basics for where the consumption comes from.

[2.b.iii] generalized list of potential data dependencies. From this generalized list, select those dependencies that can be forwarded (write down the corresponding pipeline stages that will be forwarding and receiving the data), and those dependencies that will require hazard stalls.

All data hazards we need to handle for this project essentially concern Data Production followed immediately by consumption from the data location that just had a produced value. Forwarding from the dmem out to the EXE stage can allow an instruction to move into exe right behind the producing instruction instead of waiting in the ID stage to let

the instruction before it gets to the WB stage. Forwarding could also allow any ALU instruction's result to be brought back to the ALU earlier than it would be if they had to wait for its writeback.

[2.b.iv] global list of the datapath values and control signals that are required during each pipeline stage

IF	ID	EXE	MEM	WB
s_PC_WR_EN	ID_s_instruction	EX_s_ALUSrc	MEM_s_ALUresult	s_HaltDelay_4
IF_s_PCwriteback	ID_s_PCp4	EX_s_RT	MEM_s_RT	WB_s_WrEn
EX_s_Alt	s_RegDst	EX_s_Imm	MEM_s_MemWrite	WB_s_MemtoReg
s_PCp4	s_Jump	EX_s_RS		WB_s_ALUresult
s_NextInstAddr	s_Branch	s_ALU_B		WB_s_DmemOut
s_IMemAddr	s_BranchSel	EX_s_ALUctrl		s_RD_data
s_IF_MUX_SEL	s_JRctrl	EX_s_shamt		WB_s_RegWrDataSel
	s_JAL	s_ALUresult		WB_s_RegWrData
	s_MemRead	EX_s_Instruction		
	s_MemToReg	EX_s_PCp4		
	s_MemWrite	EX_s_Jump		
	s_ALUSrc	EX_s_Branch		
	EX_s_RegWrAddr	EX_s_JRctrl		
	MEM_s_RegWrAddr	s_Zero		
	WB_s_RegWrA	s_ALU_slt		

	ddr			
	ID_s_Instruction	EX_s_BranchSel		
	EX_s_Instruction	s_WrEnIn		
	MEM_s_Instruction	EX_s_RegWr		
	s_ID_MUX_SEL	EX_s_RegWrSel		
	s_SignSel	EX_s_Alt_MID		
	s_RegWrData1			
	s_LUI			
	s_RegWrAddr1			
	s_RegWrAddr			
	s_RegWr			
	s_RegWrData			

[2.c.i] list all instructions that may result in a non-sequential PC update and in which pipeline stage that update occurs.

- Beq
- Bne
- Jump
- Jal
- Bgez
- Bgezal
- Bgtz
- Blez
- Bltzal
- Blitz

All of the PC changes occur when these instructions hit the EXE stage of execution.

When these stages hit the instruction decode, IF and ID need to be stalled, and the IF->ID Register needs to be squashed so that any instructions behind it in IMEM do not make it into the pipeline. Essentially 1 stage needs to be flushed which results in two stages being stalled.

[illegible]

Number	Output Name	Signal Name
1	o_RegDst	s_RegDst
2	o_RegWrDataSel	s_RegWrDataSel
3	o_Jump	s_Jump
4	o_Branch	s_Branch
5	o_BranchSel	s_BranchSel
6	o_JR	s_JRctrl

7	o_JAL	s_JAL
8	o_MemRead	s_MemRead
9	o_MemtoReg	s_MemToReg
10	o_MemWrite	s_MemWrite
11	o_ALUSrc	s_ALUSrc
12	o_RegWrite	s_RegWr1
13	o_EXT	s_SignSel
14	o_RegWriteSel	s_RegWrSel
15	o_ALUOp	s_ALUctrl

[2.e – i, ii, and iii] In your writeup, show the QuestaSim output for each of the following tests, and provide a discussion of result correctness. It may be helpful to also annotate the waveforms directly.

This will be a little difficult to complete as the Hardware Scheduled Pipeline is not fully functional, and most programs cannot be executed properly.



Proj1_Base_Tests.s:

These waveforms show “Hazard_Unit,” “RegFile,” and “Instruction Memory,” as this shows the most important waves visually.

[illegible]

[illegible]

simpleBranch.s:

  

*Simple branch doesn't complete as desired due to a problem with stalling after a beq instruction.

[2.e.i] Create a spreadsheet to track these cases and justify the coverage of your testing approach. Include this spreadsheet in your report as a table.

WAR hazards should be impossible, given the structure of the pipeline. Forwarding will not be demonstrated as no functionality for it was created. Given the time, we could create a forwarding unit in the EXE stage by pulling data from the cross-stage registers and porting them to beefed-up MUXs before each input of the ALU. This would also create a need for a more involved hazard detection unit to control the forwarding unit and would also re-open the ability to experience WAR hazards in the event that forwarding was not implemented correctly.

Instruction	Hazard Type	Success?
-------------	-------------	----------

addi \$t3, \$0, 08210	None	NA
addiu \$t2, \$0, 248	None	NA
add \$t1, \$t2, \$t3	RAW	YES
addu \$t1, \$t1, \$0	RAW	YES
and \$t4, \$t3, \$t1	RAW	YES
andi \$t4, \$t3, 08210	None	NA
lui \$t5, 0x1001	None	NA
nor \$t4, \$t3, \$t1	None	NA
xor \$t4, \$t3, \$t1	None	NA
xori \$t1, \$t2, 100	None	NA
or \$t4, \$t3, \$t1	RAW	YES
ori \$t1, \$t2, 100	None (Could have one if prior didnt stall though)	NA
slt \$t1, \$t2, \$t3	None	NA
slti \$t1, \$t2, -100	None	NA
sll \$t1, \$t2, 10	None	NA
srl \$t1, \$t2, 10	None	NA
sra \$t1, \$t2, 10	None	NA
lui \$t5, 0x1001	None	NA
sw \$t1, 0(\$t5)	RAW	YES
lw \$t6, 0(\$t5)	None (Both cant hit mem at the same time)	NA
sub \$t1, \$t2, \$t3	None	NA
subu \$t1, \$t2, \$t3	None	NA

[2.e.ii] Create a spreadsheet to track these cases and justify the coverage of your testing approach. Include this spreadsheet in your report as a table.

Line	Control Hazard Present	Success?
main:	NA	NA
ori \$s0, \$zero 0x1234	No	NA
j skip	CH	YES
li \$s0 0xffffffff	Never Reached	This is correct and desired
skip:	NA	NA
ori \$s1 \$zero 0x1234	No	NA
beq \$s0 \$s1 skip2	RAW and CH	YES (for both)
li \$s0 0xffffffff	Never Reached	This is correct and desired
skip2:	NA	NA
jal fun	CH	YES
ori \$s3 \$zero 0x1234	No	NA
beq \$s0, \$zero exit	CH	FAIL but not on the CH handling. Beq just doesn't work for this instruction and branches despite the condition being false.
ori \$s4 \$zero 0x1234	Never Reached	We want this to occur.
j exit	CH BUT NEVER REACHED	Would be handled appropriately if it were to be reached.
fun:	NA	NA
ori \$s2 \$zero 0x1234	No	NA
jr \$ra	CH (no RAW because CH in the JAL delayed it enough to have written to \$ra)	YES
exit: halt	NA	NA

[2.f] Report the maximum frequency your hardware-scheduled pipelined processor can run at and determine what your critical path is (specify each module/entity/component that this path goes through).

FMax: 52.84mhz Clk Constraint: 20.00ns Slack: 1.08ns

As expected, Our critical path was the alu, similar to the software-enabled pipeline. The bit shifter and adder and or/ander slow things down greatly and were, therefore, the critical path (the longest cycle). The path goes through a mux for ALU_B input and then the ALU, and then the Fetch Unit.

Total (ns)	Incr (ns)	Type	Element
=====	=====	==	=====
0.000	0.000		launch edge time
3.081	3.081	R	clock network delay
3.313	0.232	uTco	reg_N:RT_Reg dffg:\G_NBit_REG:0:DFF s_Q
3.313	0.000	FF	CELL RT_Reg \G_NBit_REG:0:DFF s_Q q
3.702	0.389	FF	IC ALU_B_MUX \G_NBit_MUX:0:MUXI g_OR2 o_F~0 datab
4.127	0.425	FF	CELL ALU_B_MUX \G_NBit_MUX:0:MUXI g_OR2 o_F~0 combout
4.741	0.614	FF	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:0:ADD g_AND1 o_F datac
5.001	0.260	FR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:0:ADD g_AND1 o_F combout
5.261	0.260	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:1:ADD g_OR o_F~0 datab
5.663	0.402	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:1:ADD g_OR o_F~0 combout
5.891	0.228	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:2:ADD g_OR o_F~0 datad
6.046	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:2:ADD g_OR o_F~0 combout
6.273	0.227	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:3:ADD g_OR o_F~0 datad
6.428	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:3:ADD g_OR o_F~0 combout
6.655	0.227	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:4:ADD g_OR o_F~0 datad
6.810	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:4:ADD g_OR o_F~0 combout
7.187	0.377	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:5:ADD g_OR o_F~0 datad
7.342	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:5:ADD g_OR o_F~0 combout
7.569	0.227	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:6:ADD g_OR o_F~0 datad
7.724	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:6:ADD g_OR o_F~0 combout
7.952	0.228	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:7:ADD g_OR o_F~0 datad
8.107	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:7:ADD g_OR o_F~0 combout
8.334	0.227	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:8:ADD g_OR o_F~0 datad
8.489	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:8:ADD g_OR o_F~0 combout
8.716	0.227	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:9:ADD g_OR o_F~0 datad
8.871	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:9:ADD g_OR o_F~0 combout
9.098	0.227	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:10:ADD g_OR o_F~0 datad
9.253	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:10:ADD g_OR o_F~0 combout
9.481	0.228	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:11:ADD g_OR o_F~0 datad
9.636	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:11:ADD g_OR o_F~0 combout
9.866	0.230	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:12:ADD g_OR o_F~0 datad
10.021	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:12:ADD g_OR o_F~0 combout
10.247	0.226	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:13:ADD g_OR o_F~0 datad
10.402	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:13:ADD g_OR o_F~0 combout
10.824	0.422	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:14:ADD g_OR o_F~0 datad
10.979	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:14:ADD g_OR o_F~0 combout
11.207	0.228	RR	IC ALU_unit G_ADD_SUB \G_NBit_ADDSUB:15:ADD g_OR o_F~0 datad
11.362	0.155	RR	CELL ALU_unit G_ADD_SUB \G_NBit_ADDSUB:15:ADD g_OR o_F~0 combout

12.891	0.155	RR	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:19:ADD g_OR o_F~0 combout
13.116	0.225	RR	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:20:ADD g_OR o_F~0 datac
13.403	0.287	RR	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:20:ADD g_OR o_F~0 combout
13.629	0.226	RR	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:21:ADD g_OR o_F~0 datac
13.916	0.287	RR	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:21:ADD g_OR o_F~0 combout
14.141	0.225	RR	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:22:ADD g_OR o_F~0 datac
14.428	0.287	RR	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:22:ADD g_OR o_F~0 combout
14.657	0.229	RR	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:23:ADD g_OR o_F~0 datad
14.812	0.155	RR	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:23:ADD g_OR o_F~0 combout
15.036	0.224	RR	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:24:ADD g_OR o_F~0 datac
15.323	0.287	RR	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:24:ADD g_OR o_F~0 combout
15.552	0.229	RR	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:25:ADD g_OR o_F~0 datad
15.707	0.155	RR	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:25:ADD g_OR o_F~0 combout
15.935	0.228	RR	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:26:ADD g_OR o_F~0 datad
16.090	0.155	RR	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:26:ADD g_OR o_F~0 combout
16.317	0.227	RR	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:27:ADD g_OR o_F~0 datad
16.472	0.155	RR	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:27:ADD g_OR o_F~0 combout
16.699	0.227	RR	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:28:ADD g_OR o_F~0 datad
16.854	0.155	RR	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:28:ADD g_OR o_F~0 combout
17.080	0.226	RR	IC	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:29:ADD g_OR o_F~0 datac
17.367	0.287	RR	CELL	ALU_unit G_ADD_SUB \G_NBit_ADDSUB:29:ADD g_OR o_F~0 combout
17.777	0.410	RR	IC	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~5 datad
17.916	0.139	RF	CELL	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~5 combout
18.143	0.227	FF	IC	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~17 datad
18.293	0.150	FR	CELL	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~17 combout
18.498	0.205	RR	IC	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~18 datad
18.637	0.139	RF	CELL	ALU_unit G_MUXout \G_NBit_MUX:31:MUXI o_F~18 combout
18.885	0.248	FF	IC	EX_Fetch_Unit branchSel o_F~0 datad
19.035	0.150	FR	CELL	EX_Fetch_Unit branchSel o_F~0 combout
19.302	0.267	RR	IC	Fetch_Unit_IF g_pcreg \G_NBit_REG:8:REGI s_Q~2 datad
19.441	0.139	RF	CELL	Fetch_Unit_IF g_pcreg \G_NBit_REG:8:REGI s_Q~2 combout
21.238	1.797	FF	IC	Fetch_Unit_IF g_MUX \G_NBit_MUX:5:MUXI g_OR2 o_F~0 datac
21.519	0.281	FF	CELL	Fetch_Unit_IF g_MUX \G_NBit_MUX:5:MUXI g_OR2 o_F~0 combout
21.747	0.228	FF	IC	Fetch_Unit_IF g_MUX \G_NBit_MUX:5:MUXI g_OR2 o_F~1 datad
21.897	0.150	FR	CELL	Fetch_Unit_IF g_MUX \G_NBit_MUX:5:MUXI g_OR2 o_F~1 combout
22.102	0.205	RR	IC	Fetch_Unit_IF g_MUX \G_NBit_MUX:5:MUXI g_OR2 o_F~2 datad
22.257	0.155	RR	CELL	Fetch_Unit_IF g_MUX \G_NBit_MUX:5:MUXI g_OR2 o_F~2 combout
22.257	0.000	RR	IC	Fetch_Unit_IF g_pcreg \G_NBit_REG:5:REGI s_Q d
22.344	0.087	RR	CELL	fetchIF:Fetch_Unit_IF PCreg:g_pcreg PCdffg:\G_NBit_REG:5:REGI s_Q

Data Required Path:

Total (ns) Incr (ns) Type Element